

## LCR-Circuits

**Object:** To determine the impedance of LCR circuit.

**Apparatus Used:** resistance, inductor coil, capacitor, connecting wires, a.c. voltmeter, milli-ammeter, low voltage a.c. source.

**Formula Used:** The following formula is used for the determination of impedance of LCR circuit.

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Where,  $Z$  : impedance of LCR circuit,

$R$  : resistance

$X_L$  : Inductive reactance,


$X_C$  : Capacitive reactance

$$R = \frac{dV_R}{dI_R}, \quad X_L = \frac{dV_L}{dI_L} \quad \text{and} \quad X_C = \frac{dV_C}{dI_C}$$

$V_R$ ,  $V_L$  and  $V_C$  are the voltage across R, L and C respectively.

$I_R$ ,  $I_L$  and  $I_C$  are the currents through R, L and C respectively.

**Circuit Diagram:**

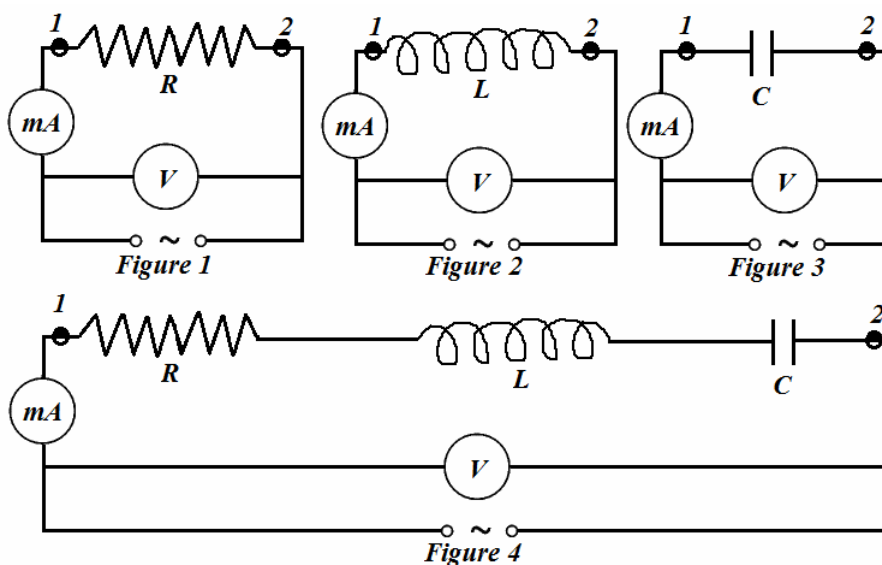

**Procedure:**

1. Note: In the given apparatus the ac. source, voltmeter and milli-ammeter are internally connected. The two points 1 and 2 are given for rest connections. So connect resistor or inductor or capacitor or series of all with points 1 and 2 to complete the circuit.
2. Initially make the circuit as shown in Figure 1. Now vary the voltage across R with help of given knob in apparatus, and note the corresponding current. This will provide you the values of  $V_R$  and  $I_R$ . Plot the graph in  $V_R$  and  $I_R$ . the slope of this graph will give the value of R.
3. Now make the circuit as shown in Figure 2. Now vary the voltage across L with help of given knob in apparatus, and note the corresponding current. This will provide you the values of  $V_L$  and  $I_L$ . Plot the graph in  $V_L$  and  $I_L$ . The slope of this graph will give the value of  $X_L$ .

- Similarly, make the circuit as shown in Figure 3. Now vary the voltage across C with help of given knob in apparatus, and note the corresponding current. This will provide you the values of  $V_C$  and  $I_C$ . Plot the graph in  $V_C$  and  $I_C$ . The slope of this graph will give the value of  $X_C$ .
- After it, make the circuit as shown in Figure 4. Now vary the voltage across combination of R, L and C with help of given knob in apparatus, and note the corresponding current. This will provide you the values of V and I. Plot the graph in V and I. The slope of this graph will give the value of Z.
- Further more calculate the value of z with the help of R,  $X_L$  and  $X_C$ . This value should be equal or approximately equal to the value of z obtained with graph.

**Observation:**

- Least count of voltmeter= ..... volts
- Least count of mili-ammeter= ..... mA
- Table for value of voltage and current

Sr.No.	R-Circuit		L-Circuit		C-Circuit		LCR-Circuit	
	$V_R$ (volt)	$I_R$ (mA)	$V_L$ (volt)	$I_L$ (mA)	$V_C$ (volt)	$I_C$ (mA)	V (volt)	I (mA)
1.								
2.								
3.								
4.								
5.								
6.								

**Calculation:**

- Show the evaluation of R,  $X_L$ ,  $X_C$  and Z with graph.
- Show the calculation of Z with the evaluated values of R,  $X_L$ , and  $X_C$ .

**Result:**

- R= .....  $\Omega$
- $X_L$ = .....  $\Omega$
- $X_C$ = .....  $\Omega$
- $Z_{graph}$ = .....  $\Omega$
- $Z_{calculated}$ = .....  $\Omega$

**Precaution:**

- Connections should be tight.
- Variation in voltage should be in slow manner.
- Reading of voltage and current should be started with zero.