

## Lecture 1: Growth and decay of current in RL circuit

### Growth of current in LR Circuit

Let us consider an inductor of self inductance  $L$  is connected to a DC source of e.m.f.  $E$  through a resistor of resistance  $R$  and a key  $K$  in series. When the key  $K$  is switched on, the current in circuit started to increase. The current in the circuit does not attain the maximum steady state value  $(E/R)$  at once because the induced e.m.f. produced across the inductor  $\left(-L \frac{dI}{dt}\right)$  opposes the growth of current. Hence the current in the circuit increases slowly to attain its steady state value.

According to KVL, the algebraic sum of instantaneous voltage drop across the circuit elements for a closed loop is zero.

Thus, for the present RL circuit,

$$\begin{aligned} E - V_1 - V_2 &= 0 \\ E &= V_1 + V_2 \end{aligned} \quad (1)$$

If at any instant the current in circuit is  $I$  then the potential drop across resistor and inductor will be  $RI$  and  $L \frac{dI}{dt}$  respectively.

Using eq.(1), we can write,

$$\begin{aligned} E &= RI + L \frac{dI}{dt} \\ E - RI &= L \frac{dI}{dt} \\ \frac{dI}{E - RI} &= \frac{1}{L} dt \end{aligned} \quad (2)$$

Integrating eq.(2)

$$\begin{aligned} \int \frac{dI}{E - RI} &= \frac{1}{L} \int dt + C' \\ -\frac{1}{R} \log_e (E - RI) &= \frac{1}{L} t + C' \end{aligned} \quad (3)$$

Here  $C'$  is integration constant and is determined by initial condition.

i.e. when  $t=0$ ,  $I=0$  then from eq.(3) we have

$$-\frac{1}{R} \log_e (E) = C' \quad (4)$$

From eqs.(3) and (4), we can write,

$$-\frac{1}{R} \log_e (E - RI) = \frac{1}{L} t - \frac{1}{R} \log_e (E)$$

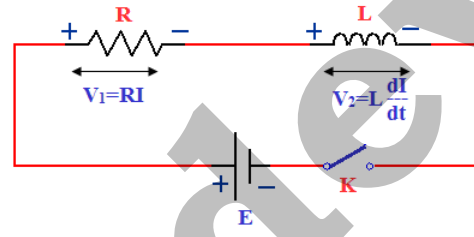


Fig 1

$$\log_e (E - RI) = -\frac{R}{L} t + \log_e (E)$$

$$\log_e (E - RI) - \log_e (E) = -\frac{R}{L} t$$

$$\log_e \frac{(E - RI)}{(E)} = -\frac{R}{L} t$$

$$\frac{E - RI}{E} = e^{-\frac{R}{L} t}$$

$$1 - \frac{R}{E} I = e^{-\frac{R}{L} t} \quad \frac{R}{E} I = 1 - e^{-\frac{R}{L} t}$$

$$I = \frac{E}{R} \left( 1 - e^{-\frac{R}{L} t} \right) \quad (5)$$

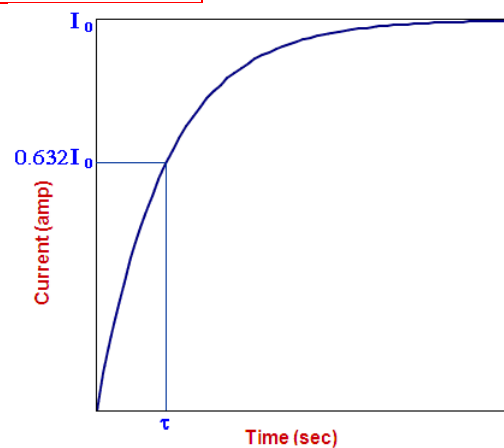


Fig.2

## Lecture 1: Growth and decay of current in RL circuit

Since, the steady state current or maximum current ( $I_0$ ) =  $E/R$

And dimension of  $L/R$  = dimension of time;

Say,  $\frac{L}{R} = \tau$  = inductive time constant

Hence eq.(4) becomes as,

$$I = I_0 \left( 1 - e^{-\frac{t}{\tau}} \right) \quad (6)$$

Eqs. (5) and (6) are called as expression of growth current in RL circuit.

These expressions indicates that-

- (1) Initially the current in the circuit is zero.
- (2) It increases exponentially following expression  $(1 - e^{-t/\tau})$ .
- (3) After infinite time current reaches to its steady state value ( $I_0$ ).

### Inductive Time constant

The Growth of current in RL circuit follows following equation.

$$I = I_0 \{ 1 - e^{-t/\tau} \}$$

When  $t = \tau$  then from above eq., we can write

$$I = I_0 \{ 1 - e^{-1} \}$$

$$I = I_0 \{ 1 - (1/e) \}$$

$$I = I_0 \{ 1 - (1/2.718) \}$$

$$I = I_0 \{ 1 - 0.368 \}$$

$$I = 0.632 I_0$$

$$I = 0.632 I_0 = 63.2\% I_0$$

Thus the time constant for the RL circuit is the time in which the current increases up to 63.2% of maximum current.

### Decay of current in LR Circuit

Let us consider a charged inductor of self inductance  $L$  is connected to a resistor of resistance  $R$  through a key  $K$  in series. When the key  $K$  is switched on, the inductor discharges through resistor. The current in circuit started to decrease due to loss of inductive energy through resistor.

According to KVL, the algebraic sum of instantaneous voltage drop across the circuit elements for a closed loop is zero.

Thus  $E - V_1 - V_2 = 0$

$$E = V_1 + V_2$$

Here  $E=0$ , Thus  $V_1 + V_2 = 0$  (1)

If at any instant the current in circuit is  $I$  then the potential drop across resistor and inductor will be  $RI$  and  $L \frac{dI}{dt}$  respectively.

Using eq.(1)

$$RI + L \frac{dI}{dt} = 0$$

$$L \frac{dI}{dt} = -RI$$

$$\frac{dI}{I} = -\frac{R}{L} dt \quad (2)$$

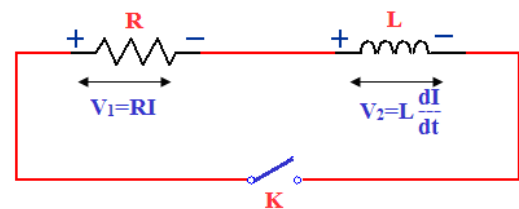


Fig.1

Integrating eq.(1)

$$\int \frac{dI}{I} = -\frac{R}{L} \int dt + C'$$

$$\log_e I = -\frac{R}{L} t + C' \quad (3)$$

Here  $C'$  is integration constant and is determined by initial condition.

i.e. when  $t=0$ ,  $I=I_0$  then from eq.(3) we have

$$\log_e I_0 = C' \quad (4)$$

From eqs. (3) and (4), we can write,

## Lecture 1: Growth and decay of current in RL circuit

$$\log_e I = -\frac{R}{L}t + \log_e I_0$$

$$\log_e \frac{I}{I_0} = -\frac{R}{L}t \quad \Rightarrow \quad \frac{I}{I_0} = e^{-\frac{R}{L}t}$$

$$I = I_0 e^{-\frac{R}{L}t} \quad (5)$$

Since, dimension of  $L/R =$  dimension of time;

Say,  $\frac{L}{R} = \tau =$  time constant

Hence eq.(5) becomes as,

$$I = I_0 e^{-t/\tau} \quad (6)$$

Eqs. (5) and (6) are called as expression for decay of current in RL circuit. These expressions indicate that Initially the current has maximum value  $I_0$  and It decreases exponentially following expression ( $e^{-t/\tau}$ ).

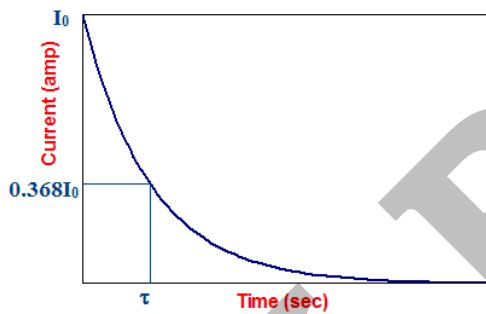


Fig.2

### Inductive Time constant

The expression for decay of current in LR circuit is

$$I = I_0 e^{-t/\tau}$$

When  $t=\tau$  then from above eq., we can write

$$I = I_0 e^{-1} = I_0 \frac{1}{e} = I_0 \frac{1}{2.718} = 0.368 I_0$$


$$I = 0.368 I_0 = 36.8\% I_0$$

Thus the time constant for the RL circuit is the time in which the current decays from steady state value to 36.8% of maximum current.

**Note A:** In the following LR circuit, when A is connected B then current rises in the circuit and inductor charges through resistor. Furthermore,

Do not publish it. Copy righted material.

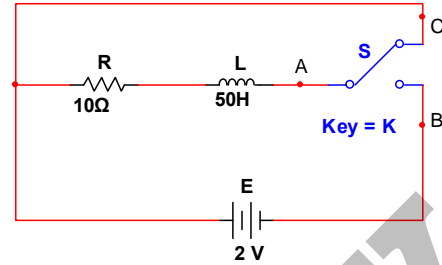when A is connected to C then the charged inductor discharges through resistor.



In the Given circuit,

Maximum current =  $I_0 = E/R = 2/10 = 0.2$  amp


Time constant =  $\tau = L/R = 50/10 = 5$  sec

The calculated growth and decay of current in the given circuit are presented in the Table A and is shown in Fig.A.

Table A

t (sec)	I <sub>growth</sub> (amp)	I <sub>decay</sub> (amp)
0	0	0.2
5	0.126424	0.073576
10	0.172933	0.027067
15	0.190043	0.009957
20	0.196337	0.003663
25	0.198652	0.001348
30	0.199504	0.000496

Fig. A

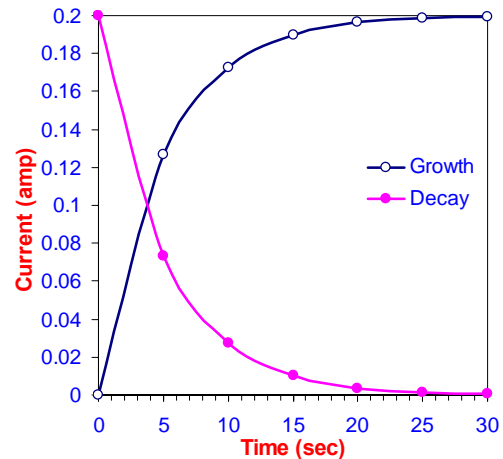

The above Table and Figure indicate that when  $t=5\tau$  then the growth current increases up to approximately maximum value  $I_0$  and decay current decreases up to zero value.

## Lecture 1: Growth and decay of current in RL circuit

**Note B:**

$$\begin{aligned} \text{Unit of } \frac{L}{R} &= \frac{\text{henry}}{\text{ohm}} = \frac{\text{volt}}{(\text{amp/sec})\text{ohm}} \\ &= \frac{\text{volt} \cdot \text{sec}}{\text{amp} \cdot \text{ohm}} = \frac{\text{volt} \cdot \text{sec}}{\text{volt}} = \text{sec} \end{aligned}$$

Dimension of  $\tau$  for LR circuit = dimension of time

**Note C:** Rate of current growth in LR circuit

$$\text{Since } I = I_0(1 - e^{-t/\tau})$$

$$\Rightarrow \frac{dI}{dt} = \frac{I_0}{\tau} e^{-t/\tau} \propto \frac{1}{\tau}$$

Hence the growth of current in LR circuit is The negative sign indicates that current decays with time.. i.e.

1. If  $\tau$ : small then current growth: fast
2. If  $\tau$ : large then current growth: slow

**Note D:** Rate of current decay in LR circuit


$$\text{Since } I = I_0 e^{-t/\tau}$$

$$\Rightarrow \frac{dI}{dt} = -\frac{I_0}{\tau} e^{-t/\tau} \propto -\frac{1}{\tau}$$

Hence the growth of current in LR circuit is inversely proportional to time constant. The negative sign indicates that current decays with time..

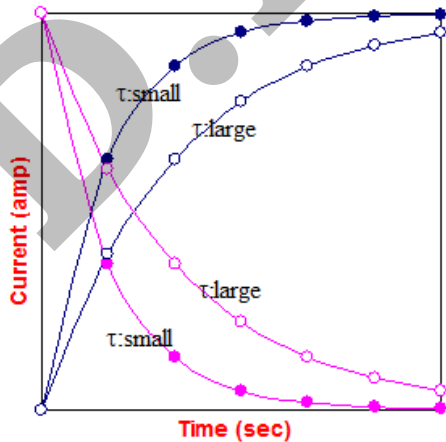1. If  $\tau$ : small then current growth: fast
2. If  $\tau$ : large then current growth: slow

**Note E:** Both growth and decay of current in LR circuit is inversely proportional to time constant.



**Example 1:** The time constant of an inductance coil is  $2.5 \times 10^{-3}$  sec. When  $60 \Omega$  resistance is added in series, the time constant reduces to  $0.5 \times 10^{-3}$  sec. Find the inductance and resistance of coil.

**Solution:** The time constant for LR circuit is  $\tau$  and after addition of  $60 \Omega$  resistance, it becomes  $\tau'$ .

$$\tau = \frac{L}{R} \quad (1)$$

$$\tau' = \frac{L}{R+60} \quad (2)$$

From eqs.(1) and (2), we have

$$\frac{\tau'}{\tau} = \frac{R}{R+60}$$

$$\frac{0.5 \times 10^{-3}}{2.5 \times 10^{-3}} = \frac{R}{R+60}$$

$$\frac{1}{5} = \frac{R}{R+60}$$

$$5R = R+60$$

$$4R = 60$$

$$R = 15 \Omega$$

Using eq.(1)

$$L = \tau R$$

$$L = 2.5 \times 10^{-3} \times 15$$

$$L = 37.5 \times 10^{-3}$$

$$L = 3.75 \times 10^{-2} \text{ henry}$$

**Example 2:** An inductor of inductance 50henry and a resister of resistance  $30 \Omega$  is connected to a d.c. source in series. Find the time in which the current reaches to half of maximum current in the circuit.

**Solution:** Given that,

$$L = 50 \text{ henry}, R = 30 \Omega, I = I_0/2 \text{ and } t=?$$

$$I = I_0(1 - e^{-Rt/L})$$

$$\frac{I_0}{2} = I_0(1 - e^{-30t/50})$$

$$\frac{1}{2} = 1 - e^{-0.6t}$$

$$e^{-0.6t} = \frac{1}{2}$$

$$e^{0.6t} = 2$$

$$0.6t = \log_e 2$$

## Lecture 1: Growth and decay of current in RL circuit

$$t = \frac{\log_e 2}{0.6} = \frac{2.3026 \log_{10} 2}{0.6}$$

$$t = \frac{2.3026 \times 0.3010}{0.6} = \frac{0.6931}{0.6}$$

$$t = 1.155 \text{ sec}$$

**Example 3:** An inductor of inductance 40henry and a resistor of resistance 10Ω is connected to a d.c. source of 6volts. Find the current after 4 sec.

**Solution:** Given that,

$E=6 \text{ volts}, L=40 \text{ henry}, R=10 \Omega, t=4 \text{ sec}, I=?$

$$I = \frac{E}{R} (1 - e^{-Rt/L}) = \frac{6}{10} (1 - e^{-10 \times 4 / 40})$$

$$I = 0.6 (1 - e^{-1}) = 0.6 \left(1 - \frac{1}{e}\right)$$

$$I = 0.6 \times \left(1 - \frac{1}{2.713}\right) = 0.6 \times (1 - 0.368)$$

$$I = 0.6 \times 0.632$$

$$I = 0.379 \text{ amp}$$

**Example 4** In an LR circuit with source, the current reaches to one third of its maximum value within 5sec. Find the time constant of the circuit.

**Solution:** Given that,  $I=I_0/3, \tau=?$

$$I = I_0 (1 - e^{-t/\tau})$$

$$\frac{I_0}{3} = I_0 (1 - e^{-t/\tau})$$

$$\frac{1}{3} = (1 - e^{-t/\tau})$$

$$e^{-t/\tau} = 1 - \frac{1}{3} = \frac{2}{3} \Rightarrow e^{t/\tau} = \frac{3}{2}$$

$$\frac{t}{\tau} = \log_e \left(\frac{3}{2}\right) = 2.3026 \times \log_{10} \left(\frac{3}{2}\right)$$

$$\frac{t}{\tau} = 2.3026 \times (\log_{10} 3 - \log_{10} 2)$$

$$\frac{t}{\tau} = 2.3026 \times (0.4771 - 0.3010)$$

$$\frac{t}{\tau} = 2.3026 \times (0.1761) = 0.4055$$

$$\tau = \frac{t}{0.4055} = \frac{5}{0.4055} = 12.33 \text{ sec}$$

$$\tau = 12.33 \text{ sec}$$

**Example 5** A resistor of 5 Ω and an inductor of 4henry is connected to source of 10 volt in series. Find the time in which current in circuit becomes 1amp.

**Solution:** Given that,  $R=5 \Omega, L=4 \text{ henry}, E=10 \text{ volts}$   
 $I=1 \text{ amp}, t=?$

$$I = \frac{E}{R} (1 - e^{-Rt/L})$$

$$1 = \frac{10}{5} (1 - e^{-5 \times t / 4})$$

$$\frac{1}{2} = 1 - e^{-5 \times t / 4}$$

$$e^{-5 \times t / 4} = 1 - \frac{1}{2} = \frac{1}{2}$$

$$e^{5 \times t / 4} = 2$$

$$\frac{5t}{4} = \log_e 2 = 2.3026 \log_{10} 2$$

$$t = \frac{4}{5} \times 2.3026 \times 0.3010 = 0.8 \times 0.6931$$

$$t = 0.554 \text{ sec}$$

**Example 6** A charged inductor of 40henry discharges through a resistor of 5Ω. Find the time in which current decays to 36.8% of its maximum current.

**Solution:** Given that,  $R=5 \Omega, L=40 \text{ henry},$   
If  $I=36.8\% I_0, t=?$

We know that when  $I=36.8\% I_0, t=\tau$

$$t = \tau = L/R = 40/5 = 8$$

$$t = 8 \text{ sec}$$

**Example 7** The time constant for a RL circuit is 5sec. In case of decay of current, find the time in which current decays to half of its maximum.

**Solution:** Given that,  $\tau = 5 \text{ sec}, I=I_0/2, t=?$

$$I = I_0 e^{-t/\tau}$$

$$\frac{I_0}{2} = I_0 e^{-t/5} \Rightarrow \frac{1}{2} = e^{-t/5}$$

$$e^{t/5} = 2$$

$$\frac{t}{5} = \log_e 2 = 2.3026 \log_{10} 2$$

$$t = 5 \times 2.3026 \times 0.3010 = 5 \times 0.6931$$

$$t = 3.466 \text{ sec}$$